

Name: _____

CIS 351 Practice Test 2

Updated October 3, 2022


1. Explain **specifically** what makes a carry-lookahead adder faster than a ripple-carry adder of the same size.
2. Draw a nine-bit carry-select adder with 3-adder blocks. How many adders and muxes are required to build your circuit? Give the propagation delay for all of the sum bits (not just the final ones).
3. Build a 4:1 mux using logic gates.
4. Show how to build an AND gate and an OR gate out of a mux.
5. Use a Karnaugh map to simplify the following Boolean expression:

$$A'B'C'D' + A'B'C'D + A'B'CD' + A'BC'D' + A'BC'D + AB'C'D' + AB'C'D + ABCD' + ABCD$$

Remember: it should be easy to write out the truth table for an expression that is already in sum-of-products form.

6. Complete the characteristic table for the circuit shown below:

| A_n | B_n | Q_n | Q_{n+1} |
|-------|-------|-------|-----------|
| 0 | 0 | 0 | |
| 0 | 0 | 1 | |
| 0 | 1 | 0 | |
| 0 | 1 | 1 | |
| 1 | 0 | 0 | |
| 1 | 0 | 1 | |
| 1 | 1 | 0 | |
| 1 | 1 | 1 | |

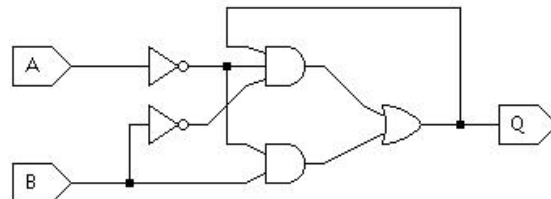


What fundamental circuit has the same characteristic table?

Name: _____

7. Complete the characteristic table for the circuit shown below: Note, there is no clock pulse here. Your answers should show the states Q and \bar{Q} after they have reached a steady state given R , S , and current values of Q and \bar{Q} . If the given inputs will produce a non-deterministic output (i.e., the output depends on which gate changes first), write “random” in the row.

| R | S | Q_{now} | \bar{Q}_{now} | Q_{next} | \bar{Q}_{next} |
|---|---|-----------|-----------------|------------|------------------|
| 0 | 0 | 0 | 0 | | |
| 0 | 0 | 0 | 1 | | |
| 0 | 0 | 1 | 0 | | |
| 0 | 0 | 1 | 1 | | |
| 0 | 1 | 0 | 0 | | |
| 0 | 1 | 0 | 1 | | |
| 0 | 1 | 1 | 0 | | |
| 0 | 1 | 1 | 1 | | |
| 1 | 0 | 0 | 0 | | |
| 1 | 0 | 0 | 1 | | |
| 1 | 0 | 1 | 0 | | |
| 1 | 0 | 1 | 1 | | |
| 1 | 1 | 0 | 0 | | |
| 1 | 1 | 0 | 1 | | |
| 1 | 1 | 1 | 0 | | |
| 1 | 1 | 1 | 1 | | |

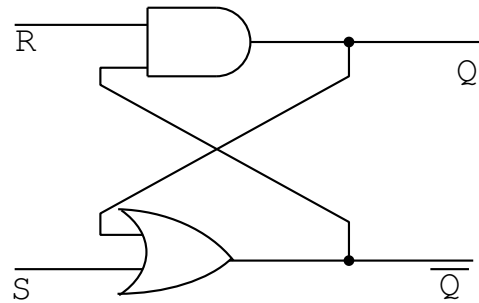

8. Choose a row labeled “random”, and explain why the output is random.
9. Review the Sequential Circuits homework.
10. Review the “golfer” example from Week 5 activities – there were several questions related to this example. (You should review the activities in general, but these ones test several skills you will need on the exam.)
11. Design a sequential circuit to run a countdown timer. This circuit should contain two registers: One for the minutes and one for the seconds. Decrement the seconds every time the clock ticks. Stop decrementing when the timer reaches 0. This circuit should have three outputs: **minutes**, **seconds**, and a one-bit **alarm** output that will be set to 1 when the timer reaches 0.